

National University of Computer and Emerging Sciences, Lahore Campus



Course:	Digital Logic Design	Course Code:	EE1005
Program:	BS(Computer Science/ Data Science)	Semester:	Spring 2023
Duration:	60 Minutes	Total Marks:	30
Paper Date:	28/02/2022	Weight	15%
Section:	ALL	Page(s):	5
Exam:	Midterm-I	Roll No.	_____
		Section:	

- Instruction/Notes:**
- Attempt all the questions on this answer booklet.
 - Make sure to write down your roll # on EVERY sheet in the given space.
 - **Use of calculator is not allowed.**

Question 1 [5+5 = 10Marks]: Number System

[CLO 1]

a) $(365)_7 + (423)_5 = (\quad \mathbf{307} \quad)_{10}$

$$\begin{aligned}
 &(365)_7 + (423)_5 \\
 &= (194)_{10} + (113)_{10} \\
 &= \mathbf{307}
 \end{aligned}$$

b) Subtract the following signed numbers using 2's complement method.

$(1010101)_2 - (1101)_2 = (\quad \mathbf{1001000} \quad)_2$

Question 2 [4 + 4 = 8 Marks]: Designing

[CLO 3]

Candidates are applying for admission in a certain degree. The passing criteria is such that the total aggregate should be greater or equal to 50%. Design a circuit that gives you an indication of the true value of the passing candidate based on below mentioned criteria.

Weightage of each parameter is as follows.

A-level result	25%
Entry test result	25%
Interview	50%

Hint: If the value of “**A level result**” is 1, it means that the candidate is able to attain 25% marks and 0 means unable to attain any mark.

(a) Fill-in the entries for the outputs in the truth table shown below:

Input			Output
A-level result	Entry test result	Interview	Pass Candidate
A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(b) Write the function F in Sum of Minterms form and Product of Maxterm form.


$$F(A,B,C) = \sum m (\text{m1, m3, m5, m6, m7})$$

$$F(A,B,C) = \prod M (\text{M0, M2, M4})$$

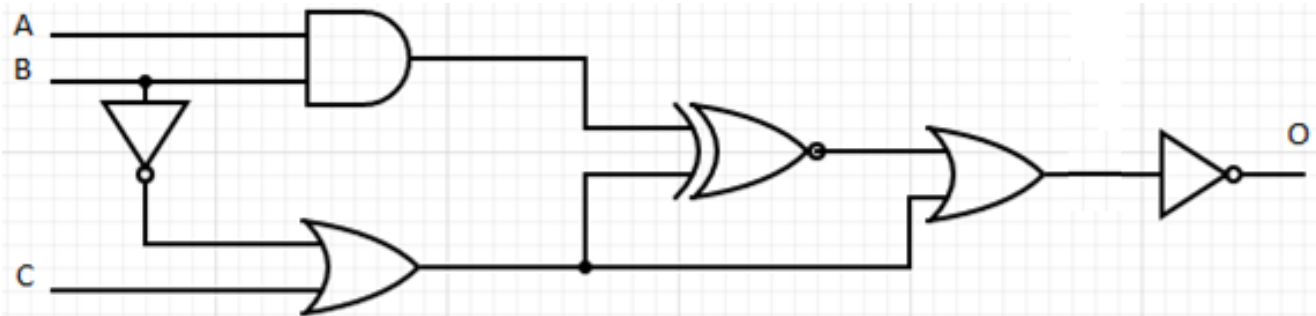Question 3 [5 Marks]: Gates

[CLO 2]

Analyze the following circuit and give its equation (no need for an optimized equation).



$$O(A, B, C) = \text{---} [[(B' + C) \oplus (A \cdot B)]' + (B' + C)]'$$

Question 4[7 Marks]: K-map Simplification

[CLO 3]

A Boolean function is given as follows:

$$F(A, B, C, D) = \prod M(4, 7, 11, 10)$$

$$\text{Don't care: } d(A, B, C, D) = \sum m(2, 3, 6, 12, 14, 15)$$

Minimize the function **F** in Product of Sums form using K-maps shown below:

CD \ AB		AB			
		00	10	11	01
00	00	0	8	X 12	0 4
	10	X 2	0 10	X 14	X 6
11	11	X 3	0 11	X 15	0 7
	01	1	9	13	5

$$F(A, B, C, D) = \text{---} C' (D + B')$$

Note: No marks will be given if K-map is not properly filled.

Rough Work