

# National University of Computer and Emerging Sciences, Lahore Campus



**Course:** Digital Logic Design  
**Program:** BS(Computer Science/ Data Science/Robotics except BSR-2E)  
**Duration:** 60 Minutes  
**Paper Date:** 10/04/2023  
**Section:** ALL  
**Exam:** Midterm-2

**Course Code:** EE1005  
**Semester:** Spring 2023  
**Total Marks:** 50  
**Weight:** 15%  
**Page(s):** 6  
**Roll No.:** \_\_\_\_\_

Solution

**Instruction/Notes:**


- Attempt all the questions in the space provided to you in this answer booklet.
- Extra rough sheets are NOT ALLOWED.
- Draw neat circuits.

**Question 1 [8 + 8 = 16 Marks]: Latches [CLO 5]**

Marks	
CLO 4 (34)	CLO 5 (16)

a) Fill in the characteristic table of A-B Latch circuit given below.

Q(t)	A	B	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

b) Fill in the reduced characteristic table of A-B Latch.

A	B	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	Q(t), Mem

## Question 2 [10+10 = 20 Marks]: Decoders and Multiplexers


Input				Output
A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Implement the function given below

$$F(A, B, C, D) = \sum m(1, 2, 3, 6, 7, 8, 11, 13, 14)$$

 - (a) Using a 4x1 MUX and external Gates only. Take A and B as Selection Inputs and C and D as Data Inputs. Properly label inputs and outputs to get credit.


$$I_0 = C + D, \quad I_1 = C, \quad \cancel{I_2 = C \odot D}, \quad I_3 = C \oplus D$$



Roll # \_\_\_\_\_

Using 3-to-8-line decoders, 1-to-2 line decoder and one NOR gate. Properly label inputs and outputs to get credit.

(b)

 



**Question 3 [14 Marks]: Design**

We have to design a machine that takes two 2-bit numbers  $A(A_1A_0)$  and  $B(B_1B_0)$  and two selection signals  $M_1M_0$  as inputs and produces result  $R$  as the output according to the following functionality:

$M_1$	$M_0$	Operation	Description
0	0	$R = A + B$	Adds A and B
0	1	$R = A - B$	Subtract B from A
1	X	$R = A * 2$	Doubles A

Your task is to make a fully functional machine. Properly show the flow of data and label all blocks and inputs/outputs to get credit.

You have to design the machine using Decoder(s) block, Adder-Subtractor(s) block and additional gates required (Detailed gate implementation of Decoder(s) blocks and Adder-Subtractor(s) blocks are not required. Also mention the sizes of decoder block and Adder/Subtractor block used) —

